

# Boolean Arithmetic

## **Usage and Copyright Notice:**

Copyright 2005 © Noam Nisan and Shimon Schocken

This presentation contains lecture materials that accompany the textbook “The Elements of Computing Systems” by Noam Nisan & Shimon Schocken, MIT Press, 2005.

We provide both PPT and PDF versions.

The book web site, [www.idc.ac.il/tecs](http://www.idc.ac.il/tecs) , features 13 such presentations, one for each book chapter. Each presentation is designed to support about 3 hours of classroom or self-study instruction.

You are welcome to use or edit this presentation as you see fit for instructional and non-commercial purposes.

If you use our materials, we will appreciate it if you will include in them a reference to the book’s web site.

If you have any questions or comments, you can reach us at [tecs.ta@gmail.com](mailto:tecs.ta@gmail.com)

# Counting systems

---

quantity	decimal	binary	3-bit register
	0	0	000
*	1	1	001
**	2	10	010
***	3	11	011
****	4	100	100
*****	5	101	101
*****	6	110	110
*****	7	111	111
*****	8	1000	overflow
*****	9	1001	overflow
*****	10	1010	overflow

$$(9038)_{ten} = 9 \cdot 10^3 + 0 \cdot 10^2 + 3 \cdot 10^1 + 8 \cdot 10^0 = 9038$$

$$(10011)_{two} = 1 \cdot 2^4 + 0 \cdot 2^3 + 0 \cdot 2^2 + 1 \cdot 2^1 + 1 \cdot 2^0 = 19$$

# Binary addition

---

- Assuming a 4-bit system:

$$\begin{array}{r} 0 \ 0 \ 0 \ 1 \\ \hline 1 \ 0 \ 0 \ 1 \\ 0 \ 1 \ 0 \ 1 \\ \hline 0 \ 1 \ 1 \ 1 \ 0 \end{array}$$

no overflow

$$\begin{array}{r} 1 \ 1 \ 1 \ 1 \\ \hline 1 \ 0 \ 1 \ 1 \\ 0 \ 1 \ 1 \ 1 \\ \hline 1 \ 0 \ 0 \ 1 \ 0 \end{array}$$

overflow

- Algorithm: exactly the same as in decimal addition
- Overflow (MSB carry) has to be dealt with.

# Representing negative numbers (4-bit system)

0	0000		
1	0001	1111	-1
2	0010	1110	-2
3	0011	1101	-3
4	0100	1100	-4
5	0101	1011	-5
6	0110	1010	-6
7	0111	1001	-7
		1000	-8

- The codes of all positive numbers begin with a "0"
- The codes of all negative numbers begin with a "1"
- To convert a number:  
leave all trailing 0's and first 1 intact,  
and flip all the remaining bits

Example:  $2 - 5 = 2 + (-5) =$

$$\begin{array}{r} 0010 \\ + 1011 \\ \hline 1101 = -3 \end{array}$$

# Building an Adder chip

---




- Adder: a chip designed to add two integers
- Proposed implementation:
  - **Half adder**: designed to add 2 bits
  - **Full adder**: designed to add 3 bits
  - **Adder**: designed to add two  $n$ -bit numbers.

# Half adder (designed to add 2 bits)

---


a	b	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

- Implementation: based on two gates that you've seen before.

# Full adder (designed to add 3 bits)

a	b	c	carry	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

- Implementation: can be based on half-adder gates.





# $n$ -bit Adder



...	1	0	1	1	a
					+
...	0	0	1	0	b
<hr/>					
...	1	1	0	1	out


- Implementation: array of full-adder gates.

# The ALU (of the Hack platform)

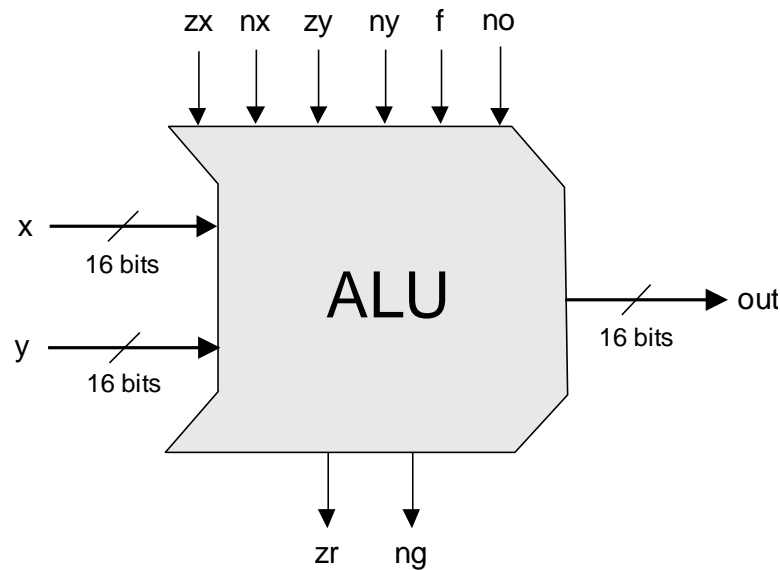 

**out(*x*, *y*, control bits) =**

***x*+*y*, *x*-*y*, *y*-*x*,**  
**0, 1, -1,**  
***x*, *y*, -*x*, -*y*,**  
***x*!, *y*!,**  
***x*+1, *y*+1, *x*-1, *y*-1,**  
***x*&*y*, *x*|*y***

 

**Chip name:** ALU

**Inputs:** x[16], y[16], // Two 16-bit data inputs  
 zx, // Zero the x input  
 nx, // Negate the x input  
 zy, // Zero the y input  
 ny, // Negate the y input  
 f, // Function code: 1 for Add, 0 for And  
 no // Negate the out output

**Outputs:** out[16], // 16-bit output  
 zr, // True iff out=0  
 ng // True iff out<0

**Function:** if zx then x = 0 // 16-bit zero constant  
 if nx then x = !x // Bit-wise negation  
 if zy then y = 0 // 16-bit zero constant  
 if ny then y = !y // Bit-wise negation  
 if f then out = x + y // Integer 2's complement addition  
 else out = x & y // Bit-wise And  
 if no then out = !out // Bit-wise negation  
 if out=0 then zr = 1 else zr = 0 // 16-bit eq. comparison  
 if out<0 then ng = 1 else ng = 0 // 16-bit neg. comparison

**Comment:** Overflow is neither detected nor handled.

These bits instruct how to preset the x input		These bits instruct how to preset the y input		This bit selects between + / And	This bit inst. how to postset out	Resulting ALU output
zx	nx	zy	ny	f	no	out=
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	f(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y


# ALU logic (Hack platform)

These bits instruct how to pre-set the x input		These bits instruct how to pre-set the y input		This bit selects between + / And	This bit inst. how to post-set out	Resulting ALU output
zx	nx	zy	ny	f	no	out=
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x And y	if no then out=!out	f (X, y) =
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1						y
0						!x
1						!y
0						-x
1						-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

Implementation: build a logic gate architecture that "reads" each control bit and does what the table specifies: if zx=1 then set x to 0, etc.

# The ALU in the CPU context (Hack platform)

out (when <b>a=0</b> )	c1	c2	c3	c4	c5	c6	out (when <b>a=1</b> )
0	1	0	1	0	1	0	
1	1	1	1	1	1	1	
-1	1	1	1	0	1	0	
D	0	0	1	1	0	0	
A	1	1	0	0	0	0	M
!D	0	0	1	1	0	1	
!A	1	1	0	0	0	1	!M
-D	0	0	1	1	1	1	
-A	1	1	0	0	1	1	-M
D+1	0	1	1	1	1	1	
A+1	1	1	0	1	1	1	M+1
D-1	0	0	1	1	1	0	
A-1	1	1	0	0	1	0	M-1
D+A	0	0	0	0	1	0	D+M
D-A	0	1	0	0	1	1	D-M
A-D	0	0	0	1	1	1	M-D
D&A	0	0	0	0	0	0	D&M
D   A	0	1	0	1	0	1	D   M

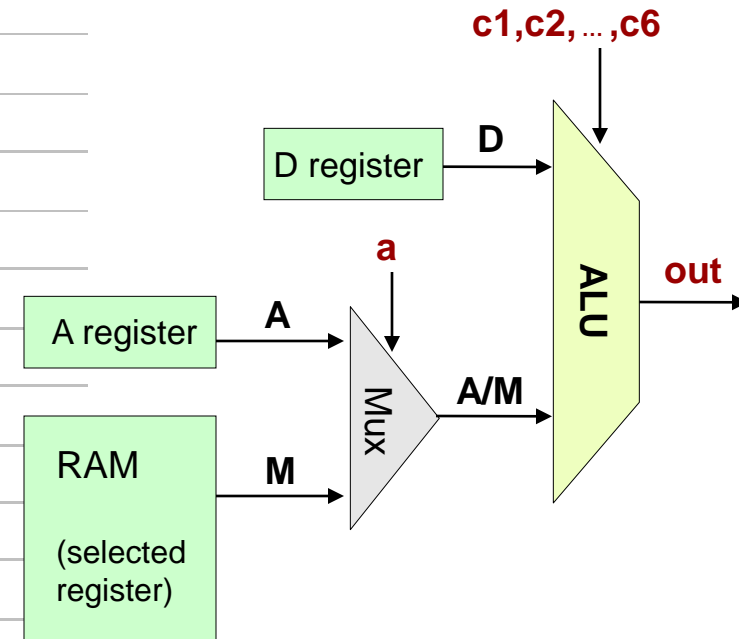

 
# Historical note: Leibnitz (1646-1716)



- "The binary system may be used in place of the decimal system; express all numbers by unity and by nothing"
- 1679: built a mechanical calculator (+, -, \*, /)



- CHALLENGE: "All who are occupied with the reading or writing of scientific literature have assuredly very often felt the want of a common scientific language, and regretted the great loss of time and trouble caused by the multiplicity of languages employed in scientific literature:
- SOLUTION: "*Characteristica Universalis*": a universal, formal, language of reasoning
- The dream's end: Turing and Goedel in 1930's.



Leibniz's medallion  
for the Duke of Brunswick

# Sequential Logic

## **Usage and Copyright Notice:**

Copyright 2005 © Noam Nisan and Shimon Schocken

This presentation contains lecture materials that accompany the textbook “The Elements of Computing Systems” by Noam Nisan & Shimon Schocken, MIT Press, 2005.

We provide both PPT and PDF versions.

The book web site, [www.idc.ac.il/tecs](http://www.idc.ac.il/tecs) , features 13 such presentations, one for each book chapter. Each presentation is designed to support about 3 hours of classroom or self-study instruction.

You are welcome to use or edit this presentation as you see fit for instructional and non-commercial purposes.

If you use our materials, we will appreciate it if you will include in them a reference to the book’s web site.

If you have any questions or comments, you can reach us at [tecs.ta@gmail.com](mailto:tecs.ta@gmail.com)



# Sequential VS combinational logic


---

- **Combinational devices**: operate on data only; provide calculation services (e.g. Nand ... ALU)
- **Sequential devices**: operate on data and a clock signal; as such, contain *state* and can be made to provide storage and synchronization services
- Sequential devices are sometimes called "clocked devices"

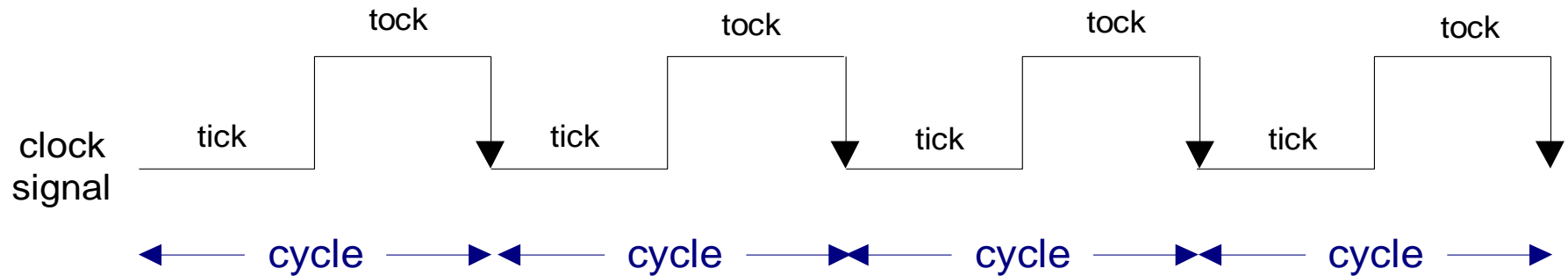
# Lecture plan

---


- Clock
- A hierarchy of memory chips:
  - Flip-flop gates
  - Binary cells
  - Registers
  - RAM
- Counters
- Perspective.



 - In our jargon, a clock cycle = *tick*-phase (low), followed by a *tock*-phase (high)
- In real hardware, the clock is implemented by an oscillator
- In our hardware simulator, clock cycles can be simulated either
  - Manually, by the user, or
  - "Automatically," by a test script.



 - A fundamental state-keeping device
- For now, let us not worry about the DFF *implementation*
- Memory devices are made from numerous flip-flops, all regulated by the same master clock signal
- Notational convention:





# 1-bit register (we call it “Bit”)



Objective: build a storage unit that can:

(a) Change its state to a given input

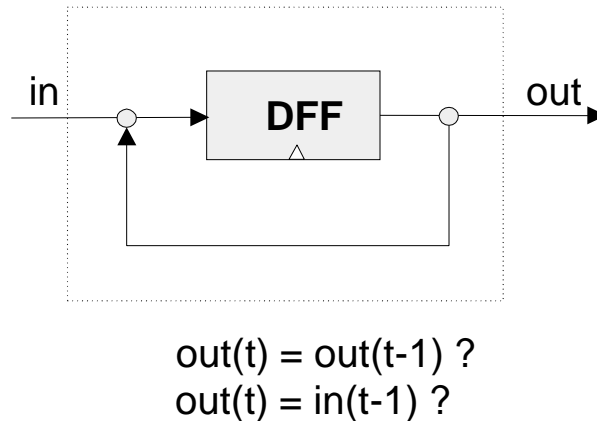 (b) Maintain its state over time (until changed)




*Won't work*

  


*OK*

## Interface

 


if  $\text{load}(t-1)$  then  $\text{out}(t) = \text{in}(t-1)$   
else  $\text{out}(t) = \text{out}(t-1)$

## Implementation

 


- Load bit
- Read logic
- Write logic

 

if  $\text{load}(t-1)$  then  $\text{out}(t)=\text{in}(t-1)$   
else  $\text{out}(t)=\text{out}(t-1)$


*1-bit register*

 

if  $\text{load}(t-1)$  then  $\text{out}(t)=\text{in}(t-1)$   
else  $\text{out}(t)=\text{out}(t-1)$

*$w$ -bit register*

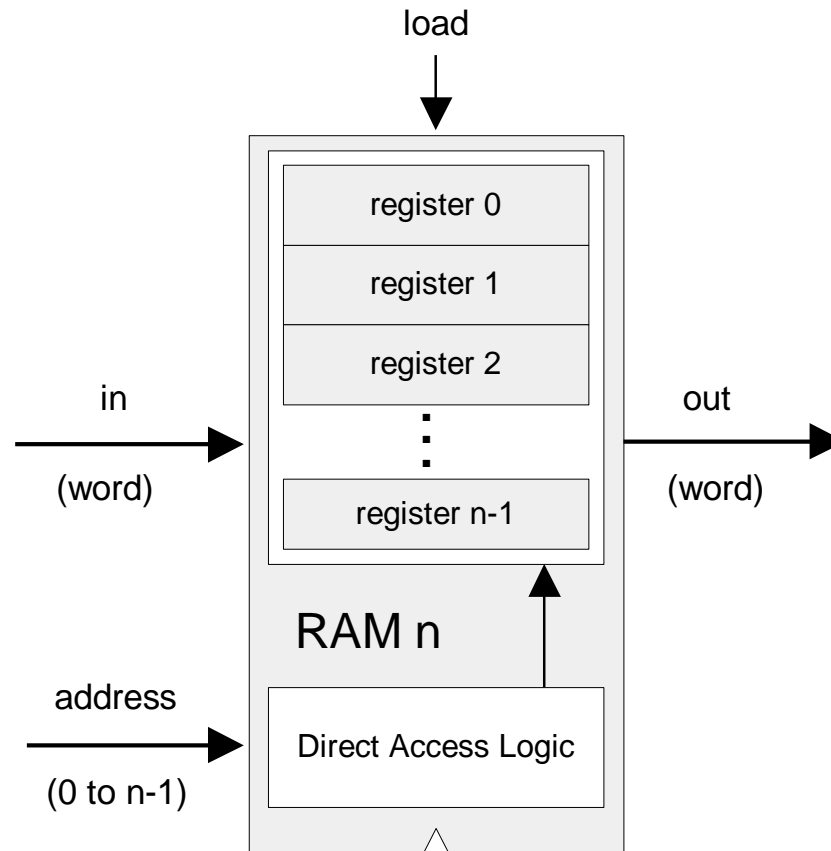
- Register's width: a trivial parameter
- Read logic
- Write logic



- Read logic
- Write logic.



# RAM interface

 


```
Chip name:  RAMn  // n and k are listed below
Inputs:     in[16], address[k], load
Outputs:    out[16]
Function:    out(t)=RAM[address(t)](t)
             If load(t-1) then
                 RAM[address(t-1)](t)=in(t-1)
Comment:    "=" is a 16-bit operation.
```

**The specific RAM chips needed for the Hack platform are:**

<u>Chip name</u>	<u>n</u>	<u>K</u>
RAM8	8	3
RAM64	64	6
RAM512	512	9
RAM4K	4096	12
RAM16K	16384	14


# RAM anatomy

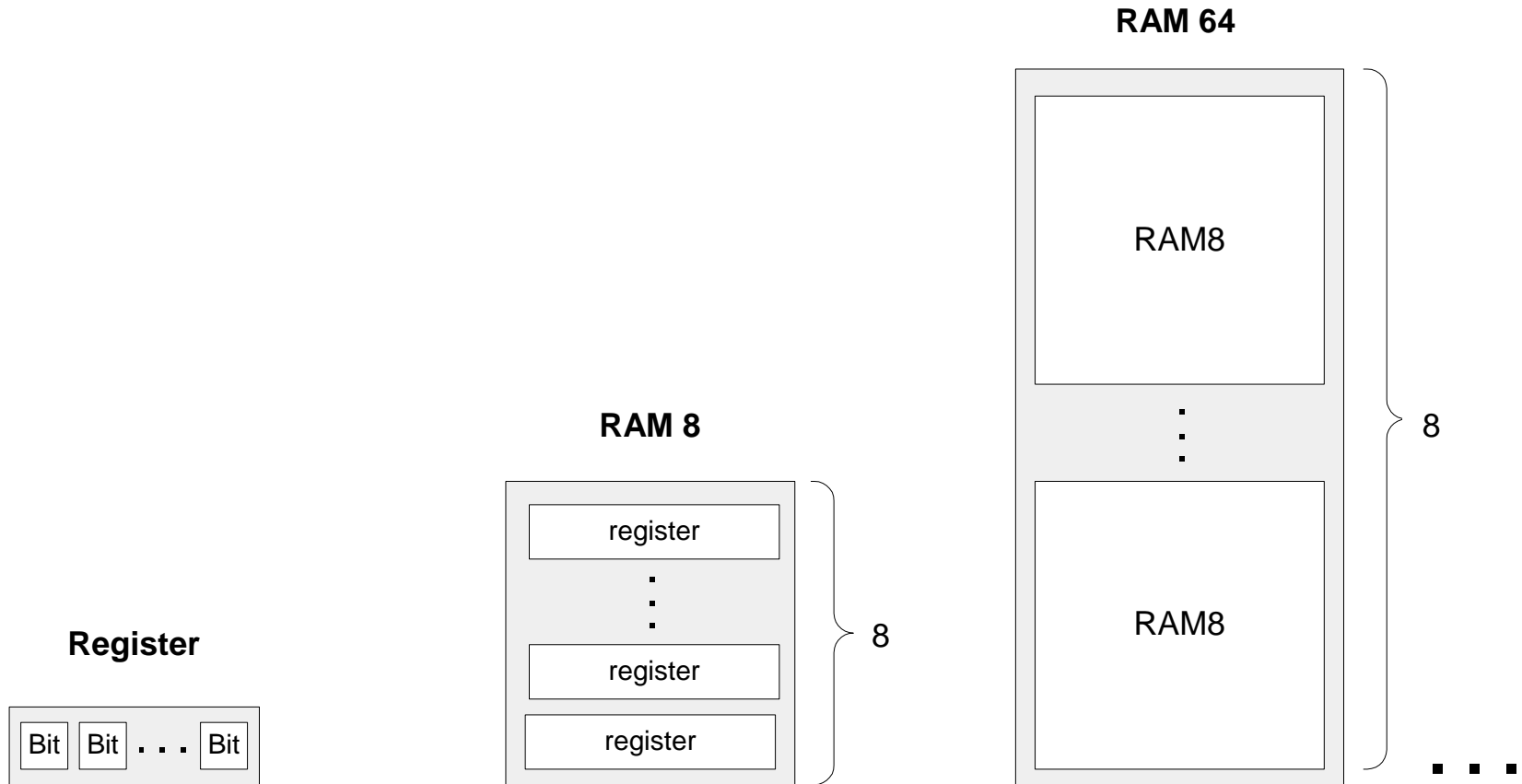

# Counter

Needed: a storage device that can:

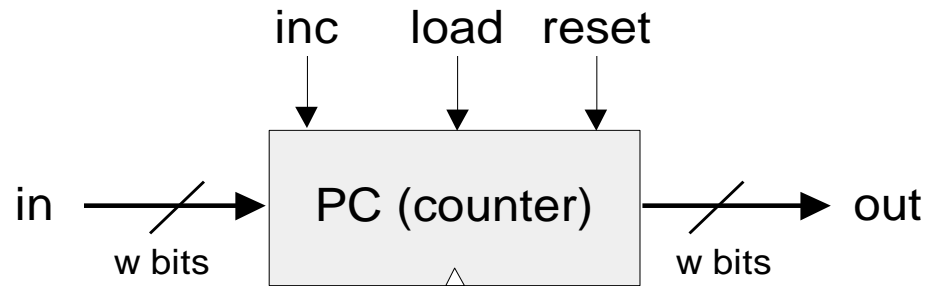- (a) set its state to some base value
- (b) increment the state in every clock cycle
- (c) maintain its state (stop incrementing) over clock cycles
- (d) reset its state




```
If reset(t-1) then out(t)=0
  else if load(t-1) then out(t)=in(t-1)
    else if inc(t-1) then out(t)=out(t-1)+1
      else out(t)=out(t-1)
```

- Typical function: *program counter*
- Implementation: register chip + some combinational logic.


# Recap: Sequential VS combinational logic

*Combinational chip*

 


$\text{out} = \text{some function of } (\text{in})$

*Sequential chip*

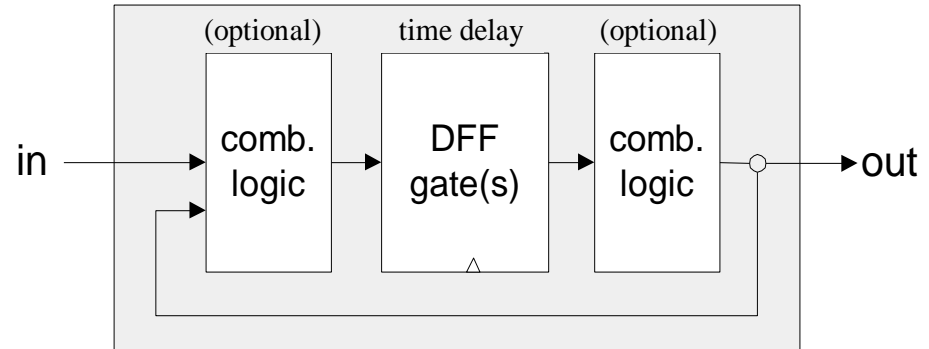


$\text{out}(t) = \text{some function of } (\text{in}(t-1), \text{out}(t-1))$

# Time matters

 

 - During a tick-tock cycle, the **internal states** of all the clocked chips are allowed to change, but their **outputs** are "latched"
- At the beginning of the next cycle, the **outputs** of all the clocked chips in the architecture **commit** to the new values.



## Implications:

- Challenge: propagation delays
- Solution: clock synchronization
- Cycle length and processing speed.

# Perspective

---

- All the memory units described in this lecture are standard

- Typical memory hierarchy


- SRAM ("static"), typically used for the cache
- DRAM ("dynamic"), typically used for main memory
- Disk

(Elaborate caching / paging algorithms)

- A Flip-flop can be built from Nand gates

- But ... real memory units are highly optimized, using a great variety of storage technologies.

Access  
time

 

Cost

